
 
 
 
 
 


How do FPGAs work?

- Basic CMOS devices
- Building gates from transistors
- Building wiring from transistors

CMOS Transistors

 - All circuit elements built from transistors of two Complementary types




Transistor Switches


TRUE = 1 = 2.3 to 3 Volts
FALSE = 0 = 0 to 0.7 Volts

1.6v is the “noise margin”


n-type

 


however:

 

p-type

 


however:


 


How do we make a better switch

 
- Transmission gate or pass gate
 - Use a switch of each type in parallel



- Alternative symbols for pass gates

  


Multiplexors

 


S	A	B	F
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

■ How do we build a 2:1 Mux?

□ Using logic gates

 

 □ Using pass gates (output ties two signals together?)




Tri-state logic

- Multiple outputs can be tied to one wire, but only if they are guaranteed to never conflict (driven simultaneously to 0 and 1)
- The “Z” state for a signal – when nothing is driving it and it is just left “floating”
- Something has to “pull it up” or “pull it down” to set a value
 - This can be gate outputs (but have to ensure they never conflict)
 - Or it can be pass outputs (but we have to ensure they never conflict)
- The difference is that pass gates can just “disconnect” by turning off – gates can’t do that


Tri-state gates

- The third value
 - ❑ logic values: “0”, “1”
 - ❑ don't care not a value: “X” (must be 0 or 1 in real circuit!)
 - ❑ third value or state: “Z” — floating, no connection
- Tri-state gates
 - ❑ additional input – output enable (OE)
 - ❑ output values are 0, 1, and Z
 - ❑ when OE is high, the gate functions normally
 - ❑ when OE is low, the gate is disconnected from wire at output
 - ❑ allows more than one gate to be connected to the same output wire
 - as long as only one has its output enabled at any one time

 


non-inverting
tri-state
buffer

In	OE	Out
X	0	Z
0	1	0
1	1	1

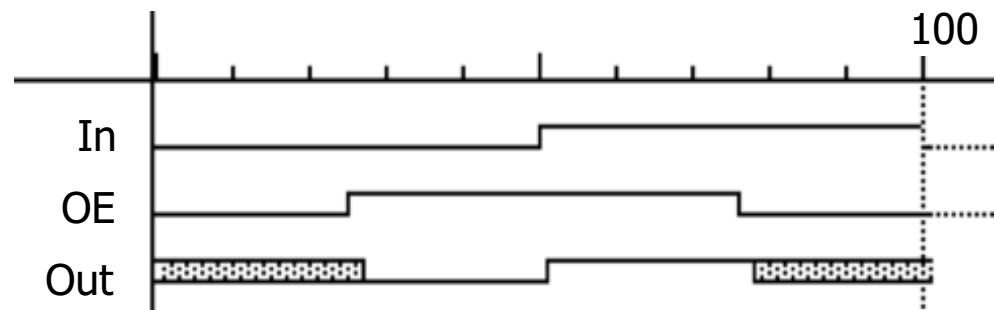



Where is tristate used?

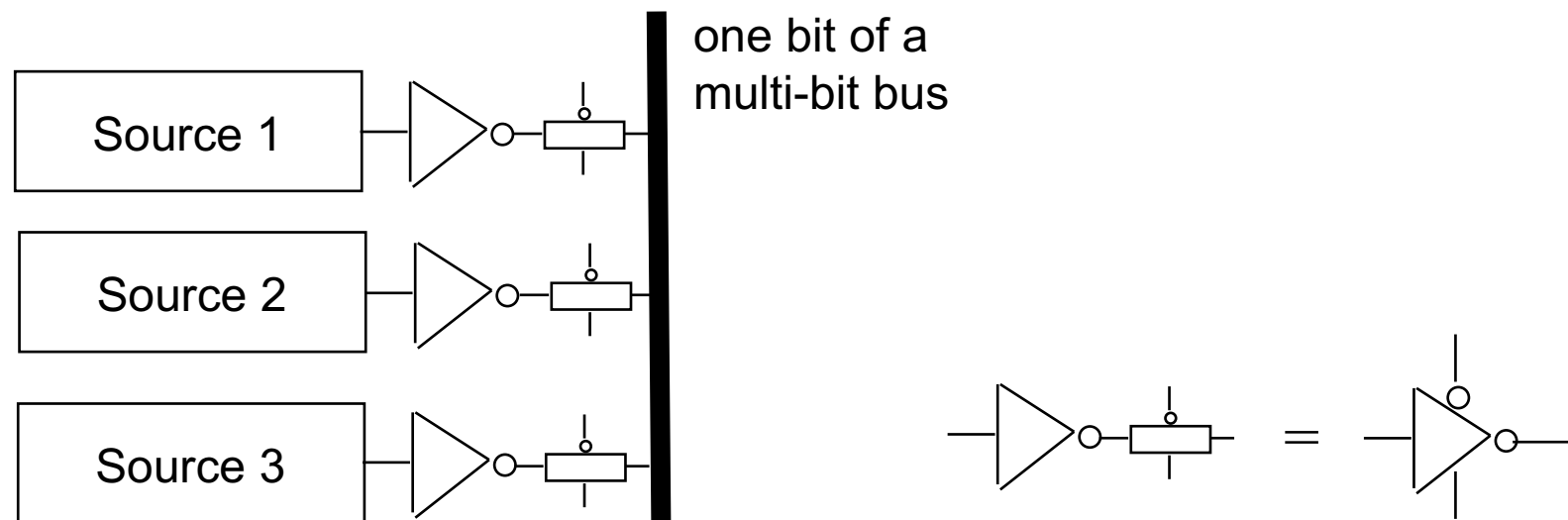- We just saw one example with a multiplexer
- Larger scale multiplexer is when we can connect many more signals onto a “bus” – a group of wires that are logically related – e.g., the output of a register such as number
- Only one pass gate can be enabled at a time
- A typical “bus” driver





Basic Gates

INV

 
 


NAND

  

		A	
		0	1
B	0	1	1
	1	1	0


NOR

  

		A	
		0	1
B	0	1	0
	1	0	0


More complex or compound gates

 - A complex boolean function can be built from basic gates (inverter, NAND, NOR)
- Alternatively, for example, $F = A'(B' + C') = (A + BC)'$ can be realized this way:





Open-collector gates and wired-AND

- Open collector: another way to connect gate outputs to the same wire
 - gate only has the ability to pull its output low
 - it cannot actively drive the wire high (default – pulled high through resistor)
- Wired-AND can be implemented with open collector logic
 - if A and B are "1", output is actively pulled low
 - if C and D are "1", output is actively pulled low
 - if one gate output is low and the other high, then low wins
 - if both gate outputs are "1", the wire value "floats", pulled high by resistor
 - low to high transition usually slower than it would have been with a gate pulling high
 - hence, the two NAND functions are ANDed together

 


Static D FF using pass gates

  - A pair of inverters can hold a value, static memory
- A value can be read, but how written?




Dynamic D FF

 - Remove feedback loop
- Must guarantee clock is frequent enough that charges stored on inputs of inverters does NOT lead away




D FF using logic gates

 

How are FPGAs built?

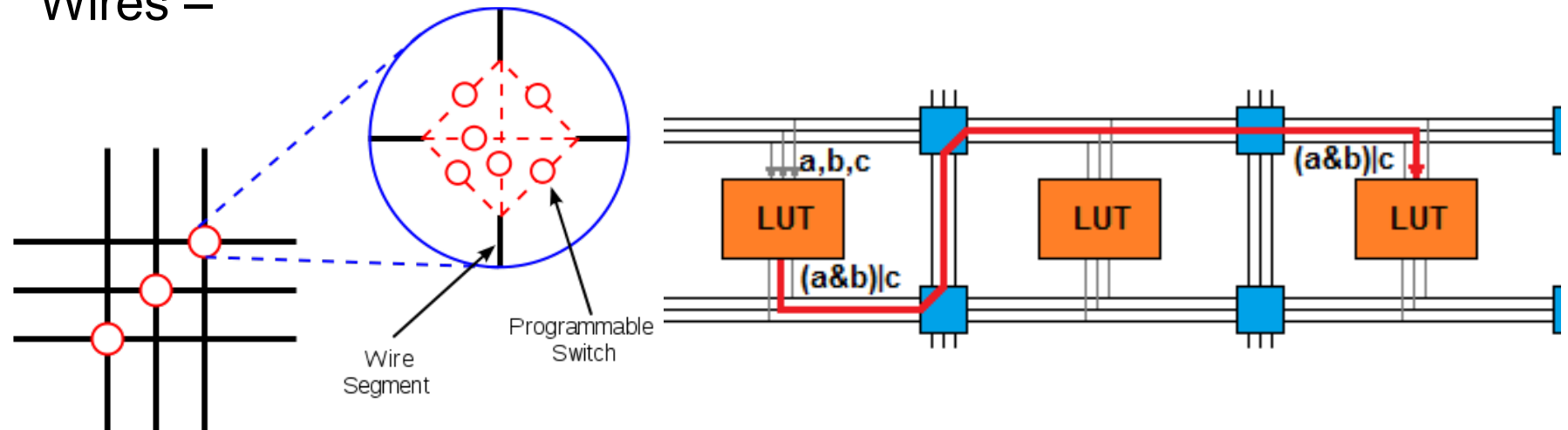- Logic - lookup tables – multiplexers (gates or pass gates)
- D-FF – static memory
- Wires –



- Programming – static memory that can be loaded with bit patterns that control inputs to LUTs and control wire connections